

Specifications:-

DC Gain = 1000 = 60dB

GBW = 50 MHz

PM ≈ 60°


slew rate =  $30 \frac{V}{\mu sec}$

$C_L = 1 pF$

Power = 400 μW

$I_{CMR(+)} = 1.6V$

$I_{CMR(-)} = 0.8V$

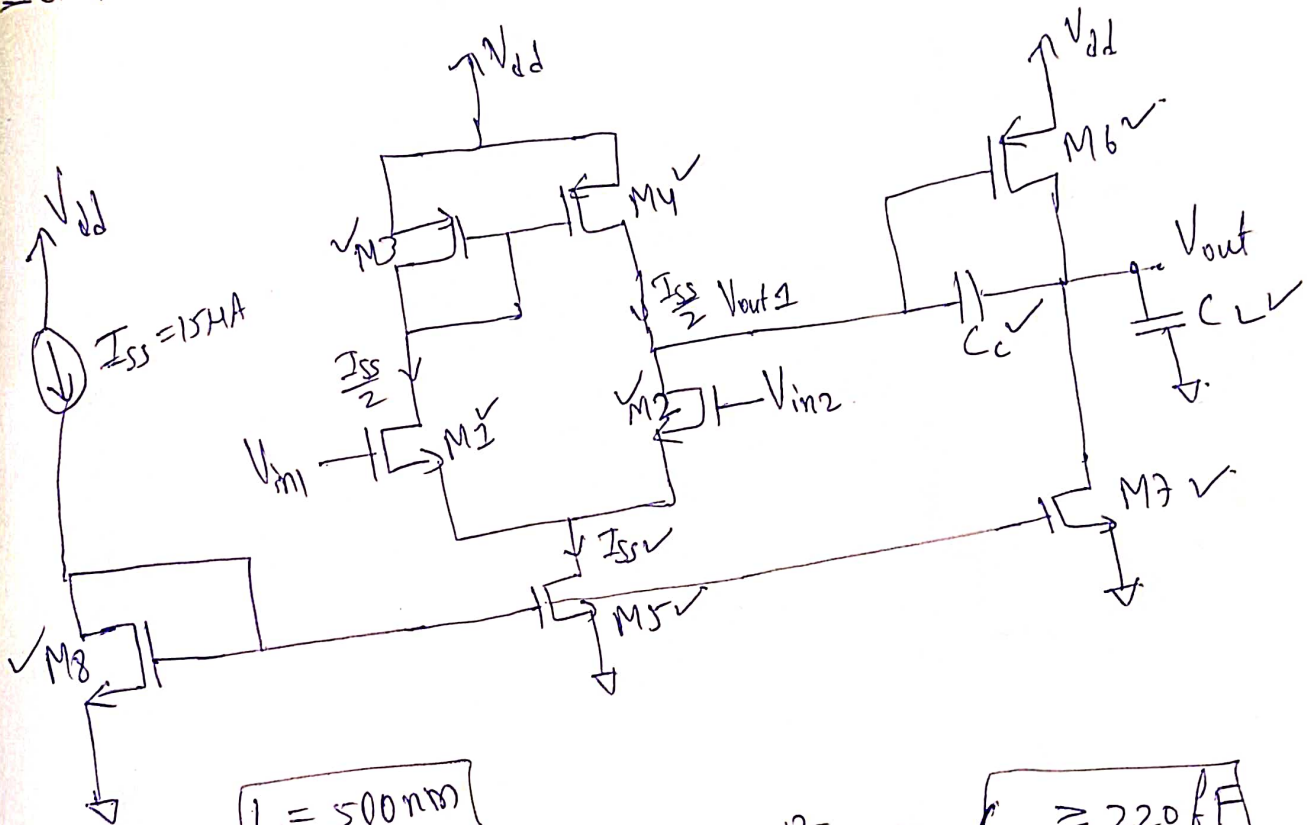

$L = 500nm$

$\Rightarrow C_c \geq 0.22 C_L \Rightarrow C_c \geq 0.22 \times 10^{-12} F \Rightarrow C_c \geq 220 fF$   
 $C_c = 500 fF$

$\Rightarrow I_{SS} = C_c SR \Rightarrow I_{SS} = 500 \times 10^{-15} \times 30 \times 10^6 \times 10^9 = 15 \times 10^{-6} = 15 \mu A$   
 $\Rightarrow I_{SS} = 15 \mu A$

M1, M2:-

$\Rightarrow (W \times BW)_w = \frac{g_{m1}}{C_c}$

$\Rightarrow 2\pi \times (GBW)_f \times C_c = g_{m1} = 2\pi \times (50 \times 10^6) \times 500 \times 10^{-15} \frac{F}{s}$   
 $g_{m1} = 157.142 \mu \frac{F}{s} \rightarrow g_{m1} = 160 \mu = g_{m2}$

$$g_{m1} = \sqrt{2 \mu_n I_1} \Rightarrow \frac{g_m^2}{2 I_1} = \mu_n C_{ox} \left( \frac{W}{L} \right)_{1,2}$$

$$\begin{aligned} V_d - V_g + V_s \\ = V_d - V_s \\ = V_{ds} - (V_g) \end{aligned}$$

$$\Rightarrow \left( \frac{W}{L} \right)_{1,2} = \frac{160 \times 160 \times 10^{-12}}{15 \times 10^{-6} \times 310 \times 10^{-6}} = 5.505 \Rightarrow \boxed{\left( \frac{W}{L} \right)_{1,2} = 6}$$

For M3, M4:

$$V_{dd} - V_{in1} = V_{sd3} + V_{dg1}$$

$$V_{dg} = V_{ds} + V_{sg}$$

$$V_{dg} = V_{ds} - V_{gs}$$

$$V_{dd} - V_{in1} = V_{sd3} + V_{ds1} - V_{gs1}$$

For M1 in Saturation:

$$V_{ds1} \geq V_{gs1} - V_{t1}$$

$$V_{ds1} - V_{gs1} \geq -V_{t1}$$

$$\Rightarrow V_{dd} - V_{in1} - V_{sd3} \geq -V_{t1}$$

$$V_{t3, \max} = 510 \text{ mV}$$

$$V_{t1, \min} = 470 \text{ mV}$$

$$\Rightarrow V_{in1} \leq V_{dd} - V_{sd3} + V_{t1}$$

$$I_{CMR}(+) = V_{dd} + V_{t1, \min} - V_{sd3, \max} \left( V_{t3, \max} + \sqrt{\frac{2 I_3}{\mu_p C_{ox} \left( \frac{W}{L} \right)}} \right)$$

$$I_{CMR}(+) = V_{dd} + V_{t1, \min} - V_{t3, \max} - \sqrt{\frac{2 I_3}{\mu_p C_{ox} \left( \frac{W}{L} \right)}}$$

$$\sqrt{\frac{2 I_3}{\mu_p C_{ox} \left( \frac{W}{L} \right)_{\min}}} = V_{dd} + V_{t1, \min} - V_{t3, \max} - I_{CMR}(+)$$

$$15 \times 10^{-6} = 160 \times 160 \times 10^{-12} \times 60 \times 10^{-6} \times \left( \frac{W}{L} \right)_{3, \min}$$

$$\left( \frac{W}{L} \right)_{3, \min} = \frac{15 \times 10^{-6}}{160 \times 160 \times 60 \times 10^{-18}} = 9.765$$

$$\Rightarrow \left( \frac{W}{L} \right)_3 \geq 9.765$$

$$g_{m3} = \sqrt{2 \times \mu_p C_{ox} \times \left( \frac{W}{L} \right)_3 \times I_D} = \sqrt{15 \times 10^{-6} \times 60 \times 10^{-6} \times 12}$$

$$\boxed{\left( \frac{W}{L} \right)_{3,4} = 12}$$

$$= 10^{-6} \times \sqrt{15 \times 12 \times 60}$$

$$\boxed{g_{m3} = 103.92 \mu}$$

For M5, M8:

$$V_{in1} = V_{gs1} + V_{ds5}$$

$$V_{ds5} \geq V_{gs5} - V_{t5}$$

$$V_{in1} - V_{gs1} \geq V_{gs5} - V_{t5}$$

$$V_{in1} \geq V_{gs1} + V_{gs5} - V_{t5}$$

$$I_{CMR(-)} = (V_{gs1} + V_{gs5} - V_{t5})_{\max} = V_{t1, \max} + \sqrt{\frac{I_{ss}}{4n\phi \times \left(\frac{W}{L}\right)_1}} + V_{t5, \max} + \sqrt{\frac{2I_{ss}}{4n\phi \times \left(\frac{W}{L}\right)_{5, \min}}} - V_{t5, \min}$$

$$(a) \quad I_{CMR(-)} = V_{gs1, \max} + \underbrace{(V_{gs5} - V_{t5})_{\max}}_{V_{ds5}} = V_{t1, \max} + \sqrt{\frac{I_{ss}}{4n\phi \times \left(\frac{W}{L}\right)_1}} + V_{ds5}$$

$$210 \text{ mV} - 590 \text{ mV} - \sqrt{\frac{15 \times 10^{-6}}{310 \times 10^{-6} \times 6}} = V_{ds5}$$

$$V_{ds5} = 210 \text{ mV} - 89.8 \text{ mV} = 120.2 \text{ mV}$$

$$I_{ss} = \frac{4n\phi \times \left(\frac{W}{L}\right)_5}{2} (V_{gs} - V_t)^2 \Rightarrow \frac{2I_{ss}}{4n\phi \times \left(\frac{W}{L}\right)_{5, \min}} = (V_{gs} - V_t)_{\max}^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_{5, \min} = \frac{2 \times 15 \times 10^{-6}}{310 \times 10^{-6}} \times \frac{1}{(V_{ds5})^2} = \frac{30}{310} \times \frac{10^6}{(120.2)^2} = 6.698$$

$$\left(\frac{W}{L}\right)_5 \geq 6.698 \Rightarrow \boxed{\left(\frac{W}{L}\right)_{5,8} = 8}$$

For M6:

$$g_{m6} \geq 10g_{m1} \Rightarrow g_{m6} = 10g_{m1} = 1600 \mu$$

$$V_{gs,3} = V_{gs,4} = V_{gs,6} \Rightarrow \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{I_6}{I_4}$$



$$I_P = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right) (V_{DS} - V_t)^2 \quad , \quad g_m = \mu_p C_{ox} \left(\frac{W}{L}\right) (V_{DS} - V_t)$$

$$\Rightarrow \frac{g_{m6}}{g_{m4}} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} \Rightarrow \left(\frac{W}{L}\right)_{6,min} = \frac{1600 \mu \times 12}{g_{m4}}$$

$$g_{m4} = \sqrt{2 \beta I} = \sqrt{2 \times \mu_p C_{ox} \times \left(\frac{W}{L}\right)_4 \times 7.5 \times 10^{-6}} = \sqrt{15 \times 10^{-6} \times 60 \times 10^{-6} \times 1}$$

$$= 10^{-6} \times \sqrt{10800} = 103.923 \times 10^{-6}$$

$$\boxed{g_{m4} = 104 \mu}$$

$$\Rightarrow \left(\frac{W}{L}\right)_{6,min} = \frac{1600 \mu \times 12}{104 \mu} = 184.615$$

$$\boxed{\left(\frac{W}{L}\right)_6 = 190}$$

~~For M2, M3~~ For M2, M3

$$\frac{I_6}{I_4} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{190}{12} \Rightarrow I_6 = \frac{190}{12} \times 7.5 \times 10^{-6}$$

$$\boxed{I_6 = 118.75 \mu}$$

$$\frac{I_5}{I_7} = \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_7} \Rightarrow \frac{15 \mu A}{118.75 \mu A} = \frac{8}{\left(\frac{W}{L}\right)_7} \Rightarrow \left(\frac{W}{L}\right)_7 = \frac{8 \times (118.75)}{15}$$

$$\left(\frac{W}{L}\right)_7 = 63.33 \Rightarrow \boxed{\left(\frac{W}{L}\right)_7 = 64}$$

~~M5, M6~~ M5, M8

$$\rightarrow \frac{4 \mu}{0.5 \mu}$$

$$M6 \rightarrow \frac{95 \mu}{0.5 \mu}$$

$$M3, M4 \rightarrow \frac{6 \mu}{0.5 \mu}$$

$$M7 \rightarrow \frac{32 \mu}{0.5 \mu}$$

$$M1, M2 \rightarrow \frac{3 \mu}{0.5 \mu}$$

$$724 \mu \rightarrow 0.7$$

$$10.3 \mu$$

Result 1:  $[C_c = 250 \text{ pF}]$

~~PM = 52°~~,  $BW \approx 53 \text{ MHz}$ ,  $\text{gain} \approx 64 \text{ dB}$   
(X) (✓)

~~$\theta = -52^\circ$~~   $\theta = -127^\circ$

PM = 53° (X).

~~PM = 52°~~

Result 2:

$[C_c = 230 \text{ pF}]$

$\theta \approx -130^\circ$ ,  $BW = 57 \text{ MHz}$ ,  $\text{gain} \approx 64 \text{ dB}$   
(X) (✓)

~~PM = 52° + 180° + 0°~~  $PM = \theta + 180^\circ = 180^\circ - 130^\circ = 50^\circ$

PM = 50° (X)

→ observed  $g_{m1,2} = 117.7 \mu$  → increased to  $146 \mu$   $\left[ \text{New } \left( \frac{W}{L} \right)_{1,2} = \frac{8.5 \mu}{0.5 \mu} \right]$

→ observed  $g_{m3,4} = 87.9 \mu$  → ~~increase~~ increased to  $95 \mu$  → then gain drastically dropped to 42 dB, so got them back

→ For  $M5, M7, M8$  → increased  $L$  to  $1 \mu\text{m}$  → gain increased by 3 dB, from 65 dB to 68 dB.  
 $\left( \frac{W}{L} \right)$  same

⇒ BW increased

But PM ↓. ( $\sim 45^\circ$ )

→ so need to move  $P2$  to right ⇒  $g_{m6}$  has to be increased.

$$g_{m6} = \sqrt{2 \beta I}$$

limit reached.

→ can't go  $w$  beyond  $100 \mu$

→ tried with  $L = L_{\min} = 180 \text{ nm}$  → but  $\gamma_{os}$  dropped and gain dropped to 20 dB.

→ When  $C_L \rightarrow 15 \text{ pF}$  from  $1 \text{ pF}$   
 $BW \uparrow$ ,  $PM \uparrow (\sim 64^\circ)$   
(X) (✓)

→ ~~increase~~ When  $C_c \rightarrow 10 \text{ pF}$  from  $250 \text{ pF}$ ,  $BW \uparrow$  to  $190 \text{ MHz}$ , But  $PM \downarrow (\sim 30^\circ)$   
with  $C_L \rightarrow 15 \text{ pF}$



## After Tuning:-

→ For  $M5, M7, M8 \rightarrow L = 1 \mu\text{m} \rightarrow (\frac{W}{L})$  same  $\rightarrow$  Because  $g_{ds7}$  was high  $\Rightarrow$  gain was low.

→ To increase BW  $\rightarrow I_{SS} = 20 \mu\text{A}$  from  $15 \mu\text{A}$ .

→ For good PM and BW  $\rightarrow C_C = 325 \text{ fF}$

→ Obtained  $SR = \frac{I_{SS}}{C_C} = \frac{20 \mu\text{A}}{325 \text{ fF}} = 61.5 \frac{\text{V}}{\mu\text{sec}}$

→ At  $V_{in} = I_{CMR(1)} :-$

$$\text{DC Gain} = 67.5781 \text{ dB}$$

$$\text{Bandwidth} = 53 - 54 \text{ MHz}$$

$$\text{PM} = 57.5568 \text{ deg}$$

$$I = 19.01 \mu\text{A} + 173.6 \mu\text{A}$$

$$P = (192.61 \mu\text{A}) \times 1.8 \text{ V}$$

$$\therefore P = 346.698 \mu\text{W}$$

→ At  $V_{in} = 1.2 \text{ V} :-$

$$\text{DC Gain} = 65.5928 \text{ dB}$$

$$\text{Bandwidth} = 56 - 57 \text{ MHz}$$

$$\text{PM} = 56.5794 \text{ deg}$$

$$I = 20.23 \mu\text{A} + 180.3 \mu\text{A}$$

$$P = (200.53 \mu\text{A}) \times 1.8 \text{ V}$$

$$\therefore P = 360.954 \mu\text{W}$$

→ At  $V_{in} = I_{CMR(4)} :-$

$$\text{DC Gain} = 59.0958 \text{ dB}$$

$$\text{Bandwidth} = 55 - 56 \text{ MHz}$$

$$\text{PM} = 57.434 \text{ deg}$$

$$I = 21.24 \mu\text{A} + 185.1 \mu\text{A}$$

$$P = (206.34 \mu\text{A}) \times 1.8 \text{ V}$$

$$\therefore P = 371.412 \mu\text{W}$$

→ Average Power =  $\frac{1079.064}{3} = 359.688 \mu\text{W}$

$$53.3857 \text{ MHz}$$

$$28.6412 \text{ mdB}$$

$$54.5434 \text{ MHz}$$

$$31.1331 \text{ mdB}$$

$$55.5672 \text{ MHz}$$

$$59.0958 \text{ dB}$$

$$65.5928 \text{ dB}$$